

Name: Mr. Lowe

Periods: 7-9

Dates: 3/16/20 – 3/18/20

EasyEDA Project #2: 555 Timer Flashing LED Circuit PCB Design

Design the below printed circuit board (PCB) in EasyEDA

